
# Lab 3 Report

Name: Devin Chaky UTEID: dmc4627 Section: 17015

Name: Manasvi Perisetty UTEID: mp49564 Section: 17015

# Part 1 -

i. Waveform of the Structural AND Gate:

 

# ii. Constraints File:

## Switches

## Connects pin V17 (SW0 on the board) to input a in our gate module

set\_property PACKAGE\_PIN V17 [get\_ports {a}]

## Sets the switch to use 3.3V logic

set\_property IOSTANDARD LVCMOS33 [get\_ports {a}]

## Connects pin V16 (SW1 on the board) to input b in our gate module


```
set_property PACKAGE_PIN V16 [get_ports {b}]
## Sets the switch to use 3.3V logic
       set_property IOSTANDARD LVCMOS33 [get_ports {b}]
## LEDs
## Connects the output c in our gate module to pin U16 (LED0 on-board)
set_property PACKAGE_PIN U16 [get_ports {out}]
## Sets the LED to use 3.3V logic
       set_property IOSTANDARD LVCMOS33 [get_ports {out}]
Part 2 -
   iii.
           Constraints File Code:
## Switches
# Connects pin V17 (SWO on the board) to input a in our gate module
set_property PACKAGE_PIN V17 [get_ports {right}]
# Sets the switch to use 3.3V logic
       set_property IOSTANDARD LVCMOS33 [get_ports {right}]
# Connects pin V16 (SW1 on the board) to input b in our gate module
set_property PACKAGE_PIN V16 [get_ports {left}]
# Sets the switch to use 3.3V logic
       set_property IOSTANDARD LVCMOS33 [get_ports {left}]
set_property PACKAGE_PIN W16 [get_ports {up}]
       set_property IOSTANDARD LVCMOS33 [get_ports {up}]
set_property PACKAGE_PIN W13 [get_ports {center}]
       set_property IOSTANDARD LVCMOS33 [get_ports {center}]
```

# Part 3 -


# iv. Truth Table:

์เทวิ	inz	in	( i	n0	а	6	C	d	e	f	9
0	0	0	(	)	0	0	0	0	0	0	1
0	0	0		1	1	0	0	1	1	1	J
0	0	1		0	0	0	ſ	0	0	١	0
0	0	1		1	0	0	0	0	1	1	0
O	1	(	)	0	1	0	0	1	1	0	0
0	1		0	(	0	1	0	٥	1	0	0
0	1		(	0	0	1	0	0	0	0	D
0		١	1	1	0	0	0	1	(	(	l
1		0	0	0	0	0	0	0	0	0	٥
(		0	0	1	0	0	0	ſ	J	0	0
(		0	1	0	-1	1	1	1	1	ı	1
	1	0	١	1	1	1	1	1	1	1	1
	1	1	0	0	1	ſ	ſ	(	J	١	1
	1	1	0	J	- 1	1	l	1	ſ	1	(
	1	1	1	0	1	ſ	1	1	-1	1	(
	١	1	1	1	1	(	1	ſ	1	1	1
 
# v, vi. Minimized Output Equations and K-Maps



# Gate Level Design:

 

# vii. <u>Structural Modeling Verilog Code:</u>

```
`timescale 1ns / 1ps
// module definition
module myBCD(
  input in3, in2, in1, in0, // input port declarations
  output a, b, c, d, e, f, g, ANO, AN1, AN2, AN3 // output port declarations
  );
  // internal signal declarations
  wire not3, not2, not1, not0,
    combo1, combo2, combo3, combo4,
    combo5, combo6, combo7, combo8,
    combo9, combo10, combo11, combo12,
    combo13, combo14, combo15;
  // assign value 0 to LCD to be used, 1 to rest
  assign AN0 = 0;
  assign AN1 = 1;
  assign AN2 = 1;
  assign AN3 = 1;
  // not gates for each input
  not int0 (not0, in0);
  not int1 (not1, in1);
  not int2 (not2, in2);
  not int3 (not3, in3);
```


```
// and gates for each product term
and t1 (combo1, in3, in2);
and t2 (combo2, in3, in1);
and t3 (combo3, not3, not2, not1, in0);
and t4 (combo4, in2, not1, not0);
and t5 (combo5, in2, not1, in0);
and t6 (combo6, in2, in1, not0);
and t7 (combo7, not2, in1, not0);
and t8 (combo8, not2, not1, in0);
and t9 (combo9, in2, not1, not0);
and t10 (combo10, in2, in1, in0);
and t11 (combo11, in2, not1);
and t12 (combo12, in1, in0);
and t13 (combo13, not2, in1);
and t14 (combo14, not3, not2, in0);
and t15 (combo15, not3, not2, not1);
// final output combos
or outa (a, combo1, combo2, combo3, combo4);
or outb (b, combo1, combo2, combo5, combo6);
or outc (c, combo1, combo2, combo7);
or outd (d, combo1, combo2, combo8, combo9, combo10);
or oute (e, combo2, in0, combo11);
or outf (f, combo1, combo12, combo13, combo14);
or outg (g, combo1, combo2, combo10, combo15);
```

endmodule

```
Testbench Code:
```

```
`timescale 1ns / 1ps
// testbench for myBCD module
module tb_myBCD;
  // create inputs of reg type
  reg [3:0] A;
  wire a, b, c, d, e, f, g; // make outputs wires
  // instantiate module to be simulated
  myBCD uut (.in0(A[0]), .in1(A[1]), .in2(A[2]), .in3(A[3]), // port declarations
         .a(a), .b(b), .c(c), .d(d), .e(e), .f(f), .g(g));
  initial begin
  for (A = 0; A < 4'b1111; A = A + 1) // use for loop to test all possible input combinations
    #10;
  end
endmodule
```

#### viii. Simulation Waveform

 

# ix. Constraints file:

```
#7 segment display
set_property PACKAGE_PIN W7 [get_ports {a}]
       set_property IOSTANDARD LVCMOS33 [get_ports {a}]
set_property PACKAGE_PIN W6 [get_ports {b}]
       set_property IOSTANDARD LVCMOS33 [get_ports {b}]
set_property PACKAGE_PIN U8 [get_ports {c}]
       set_property IOSTANDARD LVCMOS33 [get_ports {c}]
set_property PACKAGE_PIN V8 [get_ports {d}]
       set_property IOSTANDARD LVCMOS33 [get_ports {d}]
set_property PACKAGE_PIN U5 [get_ports {e}]
       set_property IOSTANDARD LVCMOS33 [get_ports {e}]
set_property PACKAGE_PIN V5 [get_ports {f}]
       set_property IOSTANDARD LVCMOS33 [get_ports {f}]
set_property PACKAGE_PIN U7 [get_ports {g}]
       set_property IOSTANDARD LVCMOS33 [get_ports {g}]
#set_property PACKAGE_PIN V7 [get_ports dp]
       #set_property IOSTANDARD LVCMOS33 [get_ports dp]
set_property PACKAGE_PIN U2 [get_ports {ANO}]
       set_property IOSTANDARD LVCMOS33 [get_ports {ANO}]
set_property PACKAGE_PIN U4 [get_ports {AN1}]
       set_property IOSTANDARD LVCMOS33 [get_ports {AN1}]
set_property PACKAGE_PIN V4 [get_ports {AN2}]
       set_property IOSTANDARD LVCMOS33 [get_ports {AN2}]
set_property PACKAGE_PIN W4 [get_ports {AN3}]
       set_property IOSTANDARD LVCMOS33 [get_ports {AN3}]
```